

第六次实验报告

存储器与控制器设计实验


22336313 郑鸿鑫

一．实验目的

1. 掌握调用 Xilinx 库 IP (Block Memory Generator) 实例化 ROM 的方法。
2. 掌握单周期 CPU 各个控制信号的作用和生成过程。
3. 掌握单周期 CPU 控制器的工作原理和设计方法。
4. 理解单周期 CPU 执行指令的过程。
5. 掌握取指、译码阶段数据通路、控制器的执行过程。

二．实验内容

下图为本次实验的原理图

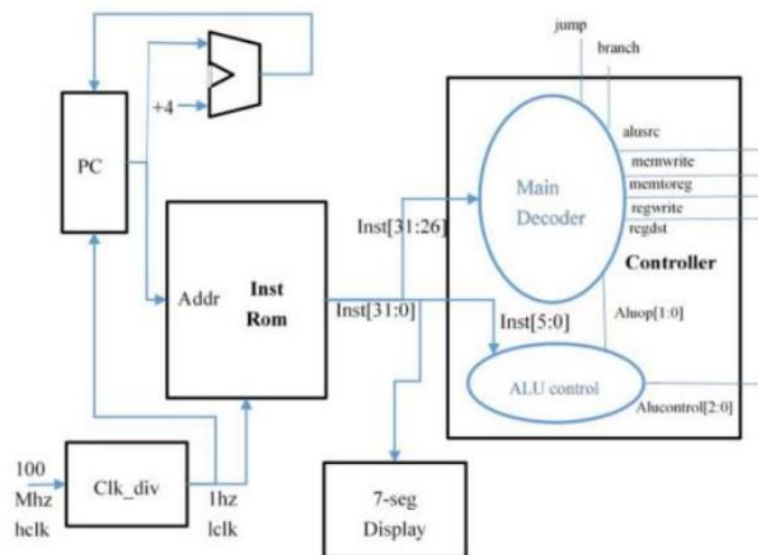

本实验实现了以下模块：

PC，用于存储 PC（一个周期），并计算下一条指令的地址；Controller，其中包含两部分 a) main_decoder，负

责判断指令类型，并生成相应的控制信号 b)


alu_decoder，负责 ALU 模块控制信号的译码，通过接收 aluop 配合 funct 字段生成 aluctr 信号；时钟分频器，将板载的 100MHz 频率降低为 1Hz，输出分频后的时钟信号；指令存储器，使用 Block Memory Generator 构造。

三 . 实验过程

1. 从存储器实验中导入 display, clk_div 模块
2. 创建 PC 模块
3. 创建 main_decoder, alu_decoder 模块
4. 创建 Controller 模块，调用 3 中的两个子模块
5. 使用 Block Memory，导入 coe 文件
6. 自定义顶层文件，连接相关模块
7. 待结果无误后，上板子进行测试

以下为模块代码展示：

模块层次

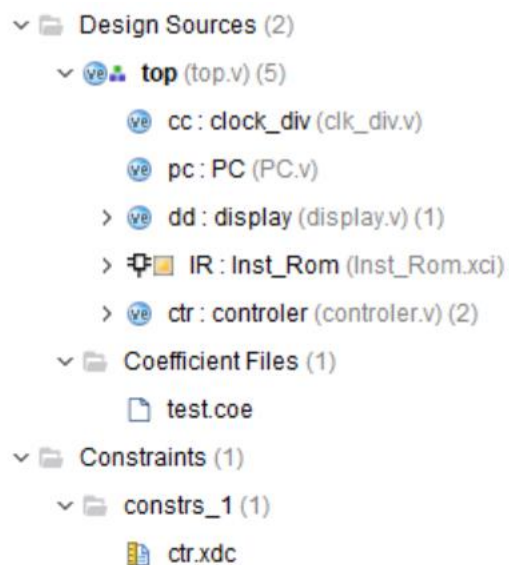

Top 文件

```
module top(
    input clk,
    input rst,
    output memtoreg,
    output memwrite,
    // output pcsrc,
    output alusrc,
    output regdst,
    output regwrite,
    output jump,
    output branch,
    output [2:0] aluctr,
    output [6:0] seg,
    output [3:0] ans
);
    wire CLK;
    wire [31:0] addre;
    wire [31:0] douta;
    // wire [31:0] naddre;
    clock_div cc(
        .clk(clk),
        .clk_sys(CLK)
    );
    PC pc(
        .clk(CLK),
        .rst(rst),
        .addre(addre)
    );
    display dd(
        .clk(clk),
        .reset(rst),
        .addra(douta[15:0]),
        .seg(seg),
        .ans(ans)
    );
    Inst_Rom IR (
        .clka(CLK), // input clka
        .addra(addre[9:2]), // input [7 : 0] addra
        .douta(douta) // output [31 : 0] douta
    );
    controler ctr(
        .op(douta[31:26]),
        .funct(douta[5:0]),
        .memtoreg(memtoreg),
        .memwrite(memwrite),
        // output pcsrc,
        .alusrc(alusrc),
        .regdst(regdst),
        .regwrite(regwrite),
        .jump(jump),
        .branch(branch),
        .aluctr(aluctr)
    );
Endmodule
```

时钟分频器代码:

```
module clock_div(
    input clk,
    output reg clk_sys = 0
);
    reg [25:0] div_counter = 0;
    always @(posedge clk) begin
        if(div_counter>=50000000) begin//上板子使用
            //if(div_counter>=50) begin//仿真使用
                clk_sys <= ~clk_sys;
                div_counter <= 0;
            end
        else begin
            div_counter <= div_counter + 1;
        end
    end
endmodule
```

PC 模块代码:

```
module PC (
    input clk,
    input rst,
    output reg [31:0] addre
);
    always @(posedge clk or negedge rst) begin
        if(rst)begin
            addre <= 32'b0;
        end
        else begin
            addre <= addre + 32'h4;
        end
    end
endmodule
```

display 模块代码, 在数码管中展示指令的低 16 位

```
module display(
    input wire clk,reset,
    input wire [15:0] addra,
    output wire [6:0]seg,
    output reg [3:0]ans
);
    reg [20:0]count;
    reg [4:0]digit;
    wire [15:0] s;
    assign s = addra[15:0];
    always@(posedge clk,posedge reset)
    if(reset)
        count = 0;
    else
        count = count + 1;
    always @(posedge clk)
    case(count[20:19])
    0:begin
        ans = 4'b1110;
        digit = s[3:0];
    end
    1:begin
```

```

        ans = 4'b1101;
        digit = s[7:4];
    end
    2:begin
        ans = 4'b1011;
        digit = s[11:8];
    end
    3:begin
        ans = 4'b0111;
        digit = s[15:12];
    end
endcase
seg U4(digit,seg);
endmodule

```

seg 模块代码（用于将 16 进制数译码到数码管显示）：

```

module seg(
    input [3:0]din,
    output reg [6:0]dout
);
always@(*)
begin
    case(din)
        4'h0:dout = 7'b000_0001;
        4'h1:dout = 7'b100_1111;
        4'h2:dout = 7'b001_0010;
        4'h3:dout = 7'b000_0110;
        4'h4:dout = 7'b100_1100;
        4'h5:dout = 7'b010_0100;
        4'h6:dout = 7'b010_0000;
        4'h7:dout = 7'b000_1111;
        4'h8:dout = 7'b000_0000;
        4'h9:dout = 7'b000_0100;
        4'ha:dout = 7'b000_1000;
        4'hb:dout = 7'b110_0000;
        4'hc:dout = 7'b011_0001;
        4'hd:dout = 7'b100_0010;
        4'he:dout = 7'b011_0000;
        4'hf:dout = 7'b011_1000;
        default:dout = 7'b000_0000;
    endcase
end
endmodule

```

controller 模块代码：

```

module controler(
    input [5:0] op,
    input [5:0] funct,
    output wire memtoreg,
    output wire memwrite,
    // output reg pcsrc,
    output wire alusrc,
    output wire regdst,
    output wire regwrite,
    output wire jump,
    output wire branch,
    output wire [2:0] aluctr

```

```

);
main_decoder mm(
    .op(op),
    .memtoreg(memtoreg),
    .memwrite(memwrite),
    //    .pcsrc(pcsrc),
    .alusrc(alusrc),
    .regdst(regdst),
    .regwrite(regwrite),
    .jump(jump),
    .branch(branch),
    .aluop(aluop)
);
alu_decoder aa(
    .funct(funct),
    .aluop(aluop),
    .aluctr(aluctr)
);
endmodule

```

main_decoder 模块代码（识别指令的 **opcode** 在生成控制信号）：

```

module main_decoder(
    input [5:0]op,
    output reg memtoreg,
    output reg memwrite,
    // output reg pcsrc,
    output reg alusrc,
    output reg regdst,
    output reg regwrite,
    output reg jump,
    output reg branch,
    output reg [1:0] aluop
);
always@(*)begin
    case(op)
        6'b000000:begin
            regwrite = 1;
            regdst = 1;
            alusrc = 0;
            branch = 0;
            memwrite = 0;
            memtoreg = 0;
            aluop = 2'b10;
        end
        6'b000010:begin
            regwrite = 0;
            memwrite = 0;
        end
        6'b100011:begin
            regwrite = 1;
            regdst = 0;
            alusrc = 1;
            branch = 0;
            memwrite = 0;
            memtoreg = 1;
        end
    endcase
end

```

```

        aluop = 2'b00;
    end
    6'b101011:begin
        regwrite = 0;
        alusrc = 1;
        branch = 0;
        memwrite = 1;
        aluop = 2'b00;
    end
    6'b000100:begin
        regwrite = 0;
        alusrc = 0;
        branch = 1;
        memwrite = 0;
        aluop = 2'b01;
    end
    6'b001000:begin
        regwrite = 1;
        regdst = 0;
        alusrc = 1;
        branch = 0;
        memwrite = 0;
        memtoreg = 0;
        aluop = 2'b00;
    end
    default: begin
        regwrite = 0;
        regdst = 0;
        alusrc = 0;
        branch = 0;
        memwrite = 0;
        memtoreg = 0;
        aluop = 2'b00;
    end
endcase
end
endmodule

```

alu_decoder 模块代码:

```

module alu_decoder (
    input [5:0]func,
    input [1:0]aluop,
    output reg [2:0] aluc,
);
    always @(*) begin
        case(aluop)
            2'b00: begin
                aluc = 3'b010;
            end
            2'b01: begin
                aluc = 3'b110;
            end
            2'b10: begin
                case(func)
                    6'b100000: aluc = 3'b010;
                    6'b100010: aluc = 3'b110;
                    6'b100100: aluc = 3'b000;

```

```

        6'b100101: alucctr = 3'b001;
        6'b101010: alucctr = 3'b111;
    endcase
end
default: alucctr = 3'b000;
endcase
end
endmodule

```

引脚分配 xdc 文件

```

# clk signal
set_property PACKAGE_PIN W5 [get_ports clk]
    set_property IOSTANDARD LVCMOS33 [get_ports clk]
    create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5}
[get_ports clk]
# leds
set_property PACKAGE_PIN U16 [get_ports memwrite]
    set_property IOSTANDARD LVCMOS33 [get_ports memwrite]
set_property PACKAGE_PIN E19 [get_ports memtoreg]
    set_property IOSTANDARD LVCMOS33 [get_ports memtoreg]
set_property PACKAGE_PIN U19 [get_ports alusrc]
    set_property IOSTANDARD LVCMOS33 [get_ports alusrc]
set_property PACKAGE_PIN V19 [get_ports regwrite]
    set_property IOSTANDARD LVCMOS33 [get_ports regwrite]
set_property PACKAGE_PIN W18 [get_ports regdst]
    set_property IOSTANDARD LVCMOS33 [get_ports regdst]
set_property PACKAGE_PIN U15 [get_ports branch]
    set_property IOSTANDARD LVCMOS33 [get_ports branch]
set_property PACKAGE_PIN U14 [get_ports jump]
    set_property IOSTANDARD LVCMOS33 [get_ports jump]
set_property PACKAGE_PIN V14 [get_ports alucctr[0]]
    set_property IOSTANDARD LVCMOS33 [get_ports alucctr[0]]
set_property PACKAGE_PIN V13 [get_ports alucctr[1]]
    set_property IOSTANDARD LVCMOS33 [get_ports alucctr[1]]
set_property PACKAGE_PIN V3 [get_ports alucctr[2]]
    set_property IOSTANDARD LVCMOS33 [get_ports alucctr[2]]

# 7 segment display
set_property PACKAGE_PIN W7 [get_ports {seg[6]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {seg[6]}]
set_property PACKAGE_PIN W6 [get_ports {seg[5]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {seg[5]}]
set_property PACKAGE_PIN U8 [get_ports {seg[4]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {seg[4]}]
set_property PACKAGE_PIN V8 [get_ports {seg[3]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {seg[3]}]
set_property PACKAGE_PIN U5 [get_ports {seg[2]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {seg[2]}]
set_property PACKAGE_PIN V5 [get_ports {seg[1]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {seg[1]}]
set_property PACKAGE_PIN U7 [get_ports {seg[0]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {seg[0]}]
set_property PACKAGE_PIN U2 [get_ports {ans[0]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {ans[0]}]
set_property PACKAGE_PIN U4 [get_ports {ans[1]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {ans[1]}]
set_property PACKAGE_PIN V4 [get_ports {ans[2]}]

```



```

set_property IOSTANDARD LVCMOS33 [get_ports {ans[2]}]
set_property PACKAGE_PIN W4 [get_ports {ans[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {ans[3]}]
##Buttons
set_property PACKAGE_PIN U18 [get_ports rst]
set_property IOSTANDARD LVCMOS33 [get_ports rst]

```

四．实验结果分析


Coe 代码如下：

```

1 memory_initialization_radix = 16;
2 memory_initialization_vector =
3 20020005,
4 2003000c,
5 2067fff7,
6 00e22025,
7 00642824,
8 00a42820,
9 10a7000a,
10 0064202a,
11 10800001,
12 20050000,
13 00e2202a,
14 00853820,
15 00e23822,
16 ac670044,
17 8c020050,
18 08000011,
19 20020001,
20 ac020054

```

模块综合后上板结果：（以前几条指令为例，且只展示低16位）

 

五 . 实验总结

实验结果符合预期，数码管显示与 coe 文件符合良好，在按下 rst 按钮后，Pc 会清零后重新从 0 地址开始读出指令。实验中遇到的问题：实现过程中数码管总是显示乱码，检查后发现，是引脚分配文件中 seg 0~6 配置反了；数码管总是只显示一位，而且本身 display 代码没有问题，检查后发现是接入的时钟是分频后的时钟导致时钟频率过低，无法进行动态扫描，改接分频前的时钟后则正常